

Circuit Diagram Description

Components:

Arduino Uno/nano

L298N Motor Driver

IR Sensors (5x) for line tracking

IR Obstacle Sensors (2x) for left/right detection

DC Motors (2x)

Potentiometer (speed control)

Push Button (start/stop)

LEDs (Red/Green) for obstacle indication

Resistors (220Ω for LEDs, 10kΩ for pull-up/down as needed)

Connections Table

Component	Arduino Pin	Details
<b>L298N Motor Driver</b>		
ENA (Enable Left)	D9 (PWM)	Left motor speed control
IN1 (Left M1)	D4	Left motor direction control
IN2 (Left M2)	D5	
ENB (Enable Right)	D10 (PWM)	Right motor speed control
IN3 (Right M1)	D6	Right motor direction control
IN4 (Right M2)	D7	
<b>Line IR Sensors</b>		
Sensor 1 (Leftmost)	A0	Detects left edge/line
Sensor 2	A1	
Sensor 3 (Center)	A2	Primary line detection
Sensor 4	A3	
Sensor 5 (Rightmost)	A4	Detects right edge/line
<b>Obstacle IR Sensors</b>		
Left Obstacle	D12	Triggers Red LED (D10)
Right Obstacle	D13	Triggers Green LED (D11)
<b>Potentiometer</b>	A5	Middle pin connected; outer pins to 5V and GND
<b>Push Button</b>	D3	Pull-up resistor to 5V, other side to GND
<b>LEDs</b>		
Red LED	D10	Anode → 220Ω resistor → D10; Cathode → GND

Component	Arduino Pin Details	
Green LED	D11	Anode → 220Ω resistor → D11; Cathode → GND
<b>Power</b>		
L298N VCC	External 9V	Separate power for motors
Arduino VIN	9V Battery	Power for Arduino (or USB)